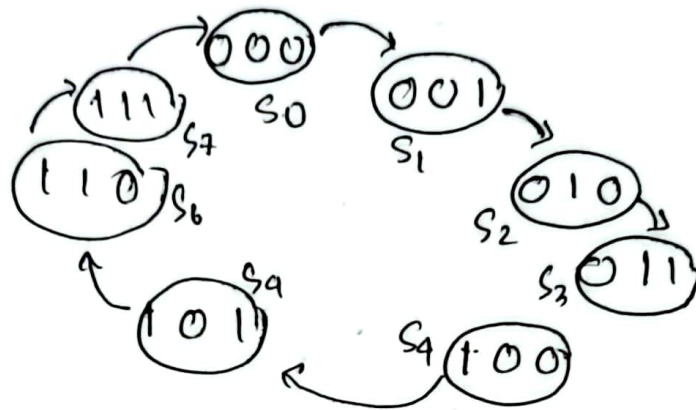


## Chosen Characters

rhym 47


### State Diagram:




### State Table: (JK-FlipFlop)

Present State			Next State			Excitation Table					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q' <sub>2</sub>	Q' <sub>1</sub>	Q' <sub>0</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1


# K-Map for JK-FlipFlops

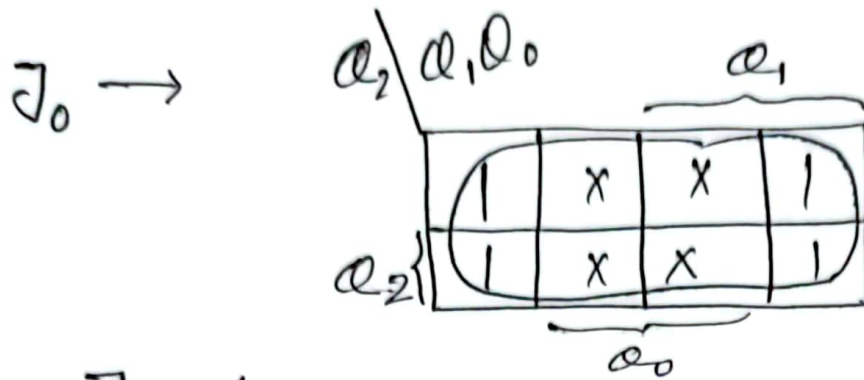


$$J_0 = 1$$

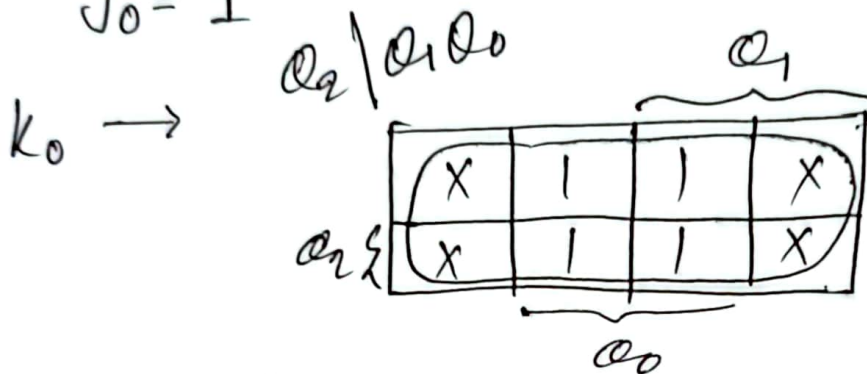

$$K_0 = 1$$

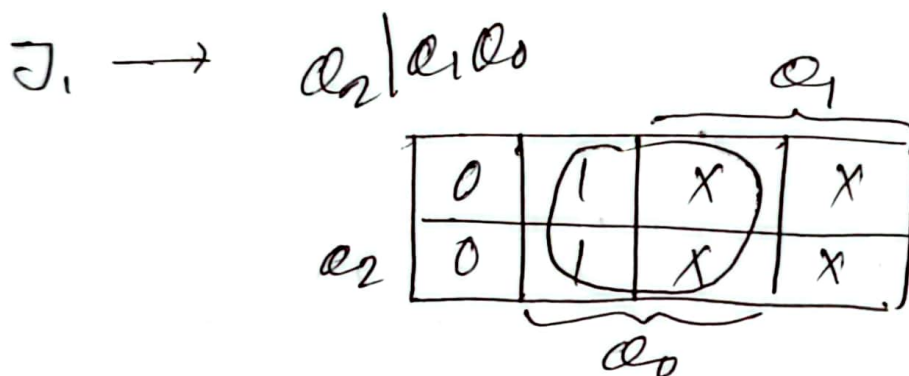

$$J_1 = Q_0$$

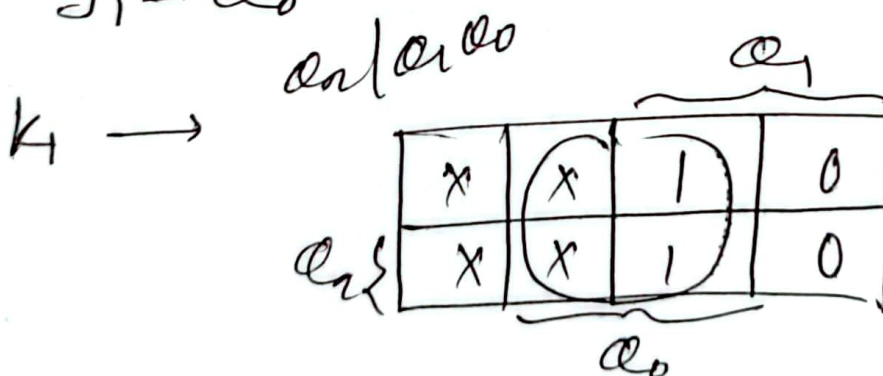

$$K_1 = Q_0$$

# State Table (T-FlipFlop)

Present State			Next State			Excitation Table		
$Q_2$	$Q_1$	$Q_0$	$Q_2'$	$Q_1'$	$Q_0'$	$T_2$	$T_1$	$T_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$T_2 \rightarrow$

$Q_2/Q_1Q_0$

	$Q_1$			
	0	0	1	0
$Q_2$	0	0	1	0
	$Q_0$			

$$T_2 = Q_1 Q_0$$

$T_0 \rightarrow$

$Q_2/Q_1Q_0$

	$Q_1$			
	1	1	1	1
$Q_2$	1	1	1	1
	$Q_0$			

$$T_0 = 1$$

$T_1 \rightarrow$

$Q_2/Q_1Q_0$

	$Q_1$			
	0	1	1	0
$Q_2$	0	1	0	1
	$Q_0$			

$$T_1 = \bar{Q}_1 Q_0 + Q_0$$


$$= Q_0 (1 + \bar{Q}_1) = Q_0$$

$$\therefore T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_1 Q_0$$

## Circuit Diagram:

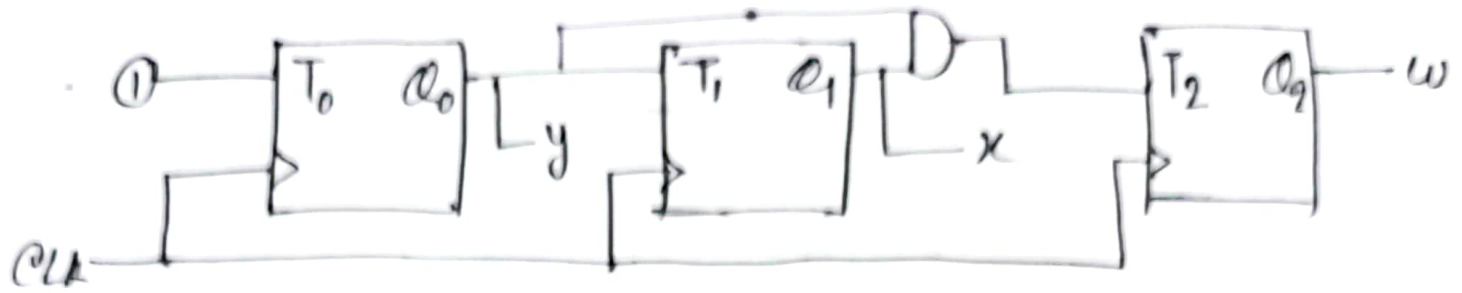



## State Table: (D Flip-Flop)

Present State			Next State			Excitation Table		
$Q_2$	$Q_1$	$Q_0$	$Q_2'$	$Q_1'$	$Q_0'$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

$$D_2 \rightarrow Q_2 / Q_1 Q_0$$

$$D_2 = Q_2(\bar{Q}_0 + \bar{Q}_1)$$

$$Q_2 / Q_1 Q_0$$

	$Q_1$		
	0	1	
$Q_2$	0	1	0
	0	1	1

$$D_1 \rightarrow Q_1 / Q_0$$

$$Q_1 / Q_0$$

	$Q_0$	
	0	1
$Q_1$	0	1
	0	1

$$D_1 = Q_1 \oplus Q_0$$


$$D_0 \rightarrow$$

$$Q_0$$

	$Q_0$	
	0	1
$Q_0$	0	1
	0	1

$$D_0 = \bar{Q}_0$$

Circuit Diagram:

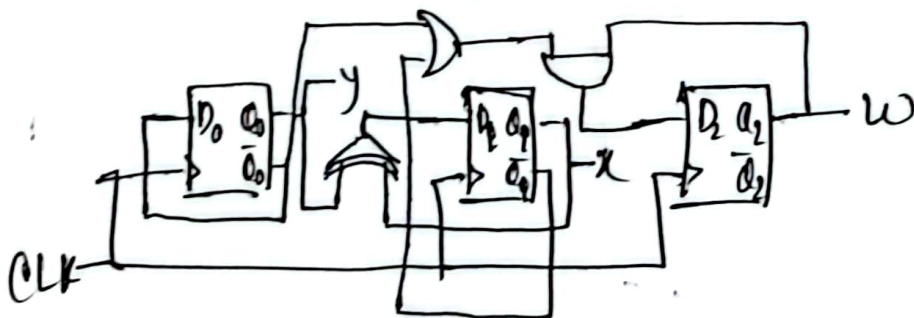

$J_2 \rightarrow a_2 | a_1 a_0$

	0	0	1	0
$a_2$	x	x	x	x

$a_1$

$a_0$

$$J_2 = a_1 a_0$$


$k_2 \rightarrow a_2 | a_1 a_0$

		$a_1$	
	x	x	x
$a_2$	0	0	1
	$a_0$		

$$k_2 = a_1 a_0$$

$$J_0 = k_0 = 1, \quad J_1 = k_1 = a_0, \quad J_2 = k_2 = a_1 a_0$$

### Circuit Diagram

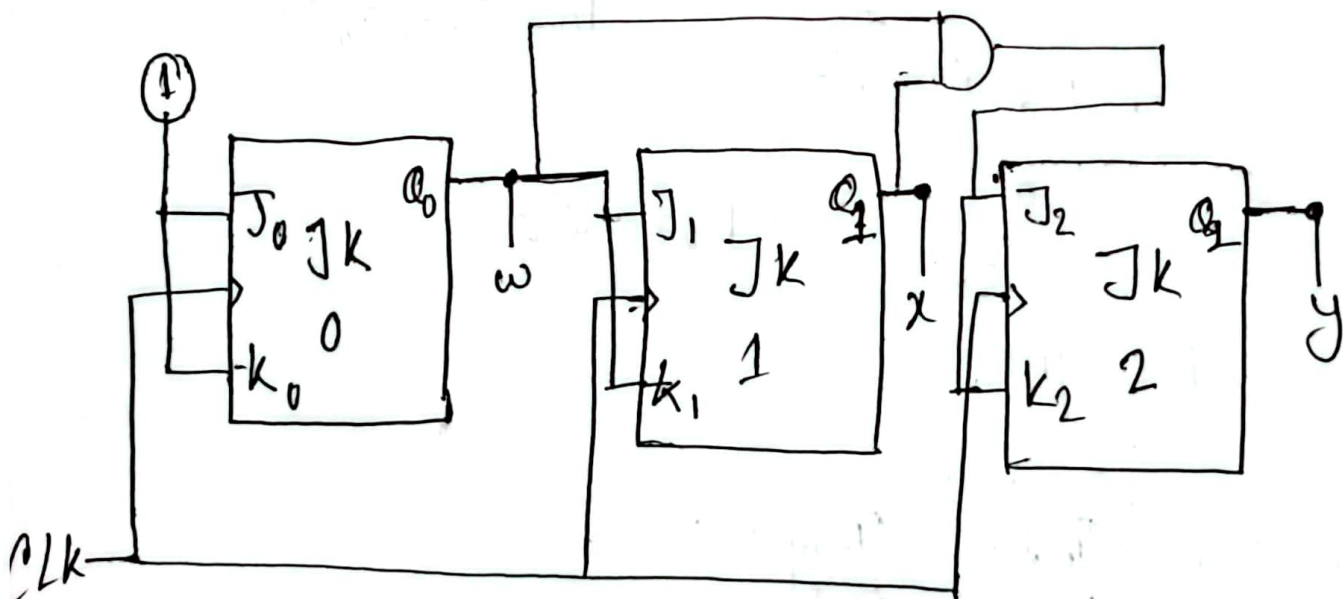

## Cost Analysis

### JK FlipFlop

JK FlipFlop gates : 3  
2 input AND gate: 1

Number of IC

JK FlipFlop (7476) : 2

Cost :  $2 \times 35 = 70 + k$

2 Input AND (7408) : 1

Cost :  $30 = 30 + k$

Total JK FlipFlop Cost =  $100 + k$

### SOM cost with JK

$$(563 + 100) = 663 + k$$

### POM cost with JK

$$(564 + 100) = 664 + k$$

### SOP cost with JK

$$(175 + 100) = 275 + k$$

### POS cost with JK

$$(292 + 100) = 392 + k$$

NAND cost with JK

$$(181 + 100) = 281 + k$$

NOR cost with JK

$$(285 + 100) = 385 + k$$

Multiplexer cost with JK

$$(128 + 100) = 228 + k$$

Decoder cost with JK

$$(185 + 100) = 285 + k$$

Cost Analysis (D-Flip Flop)

D Flip Flops : 3

X-OR gates : 1

2 Input AND gates : 2

2 Input OR gate : 1

Number of IC :

$$\text{D Flip Flop} \rightarrow (2 \times 50) = 100 + k$$

$$\text{XOR IC} \rightarrow (1 \times 25) = 25 + k$$

$$\text{AND (7408)} \rightarrow (1 \times 30) = 30 + k$$

$$\text{OR (7432)} \rightarrow (1 \times 30) = 30 + k$$

$$\text{Total D-Flip Flop cost} = 185 + k$$



SOM cost with D

$$(563 + 185) = 748 \text{ tk}$$

POM cost with D

$$(564 + 185) = 749 \text{ tk}$$

SOP cost with D

$$(175 + 185) = 360 \text{ tk}$$

POB cost with D

$$(292 + 185) = 477 \text{ tk}$$

NAND cost with D

$$(181 + 185) = 366 \text{ tk}$$

NOR cost with D

$$(285 + 185) = 470 \text{ tk}$$

MUX cost with D

$$(128 + 185) = 313 \text{ tk}$$

Decoder cost with D

$$(185 + 185) = 370 \text{ tk}$$

## Cost Analysis (T-Flip-Flops)

T FlipFlops : 3

2 Input AND : 1

IC :

T FlipFlop IC :  $(2 \times 50) = 100tk$

2 Input AND(7408) :  $(1 \times 30) = 30tk$

Total T-FlipFlop cost 130tk

SOM cost with T | POM cost with T

$$(563 + 130) = 693tk \quad | \quad (564 + 130) = 694tk$$

SOP cost with T | POS cost with T

$$(175 + 130) = 305tk \quad | \quad (292 + 130) = 422tk$$

NAND cost with T | NOR cost with T

$$(181 + 130) = 310tk \quad | \quad (285 + 130) = 415tk$$

mux cost with T | Decoder cost with T

$$(128 + 130) = 258tk \quad | \quad (185 + 130) = 315tk$$